

Analog Electronics

Experiment 2: Common source amplifier

By: Sparsh Arya

Registration number: 17BEC0656

Slot: L33+L34

Aim:

To design a common source amplifier for given specification and plot it's frequency response.

Design:

$$V_{cc} = 12V$$

$$V_{DS} = 40\% \text{ of } V_{DD}$$

$$V_{DD} = 10V$$

$$V_{DS} = 4V$$

$$R_g (R_1) = 1M\Omega$$

$$R_s = 2k\Omega$$

$$A_v = 0.9$$

$$V_{in} = 100mV$$

$$V_{gs} = 2.6V$$

$$C_s = 1/(2*\pi*(1/g_m || R_s)*f)$$

$$= 200\mu F$$

$$R_d = (V_{DD} - V_D)/I_D$$

$$= 10k\Omega$$

$$I_{DS} = (1/2)*k_n*(W/L)*(V_{gs} - V_t)^2$$



$$= 0.5mA$$

$$g_m = 2I_d/V_{ov}$$

$$= 100mV/A$$

$$C_1 = 1.6nF$$

$$C_2 = 0.22\mu F$$

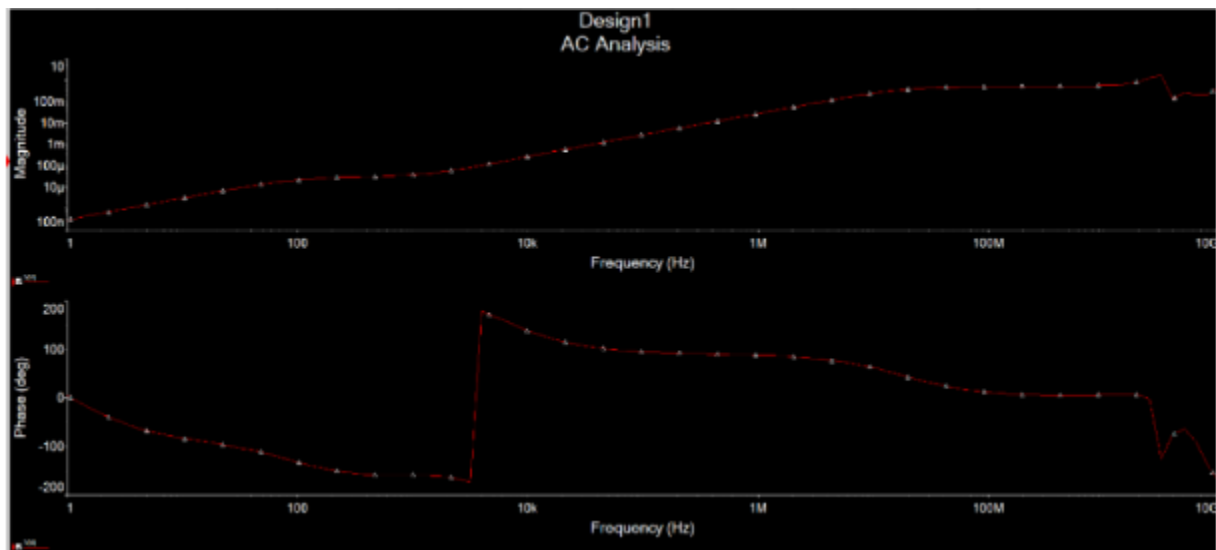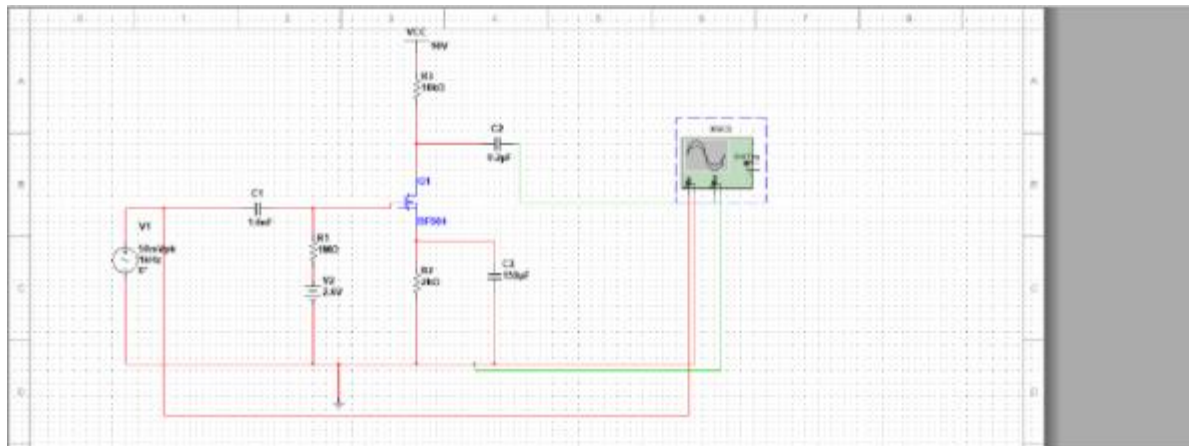

The end