

Analog Electronics

Experiment 1: CE Amplifier

By: Sparsh Arya

Registration number: 17BEC0656

Slot: L33+L34

Aim:

To design a CE amplifier for the given specifications and plot it's frequency response.

Design:

Voltage gain (A_v) = 100

$V_{CC} = 12V$

$I_C = 4mA$

$f = 100Hz$

$\beta = 200$

To find R_E : $V_{ce} = 6V$

$V_{RE} = 1.2V$

$V_{RC} = 4.8V$

To find R_1 and R_2 :

$V_{R2} = V_{BE} + V_{RE}$

$= 0.7 + 1.2$

$= 1.9$

Assume the current passing through R_1 and R_2 as $10I_B$ and $9I_B$.

$I_B = I_C / \beta = 0.02 \times 10^{-3}$

$R_2 = 10.55k\Omega$

$R_1 = 50,500k\Omega$

$R_C = 1200\Omega$



$$V_{RC} = 4.8V$$

$$R_B = 8730.62\Omega$$

$$C = 100nF$$

$$C_E = 5.3 \times 10^{-5} F$$

Output

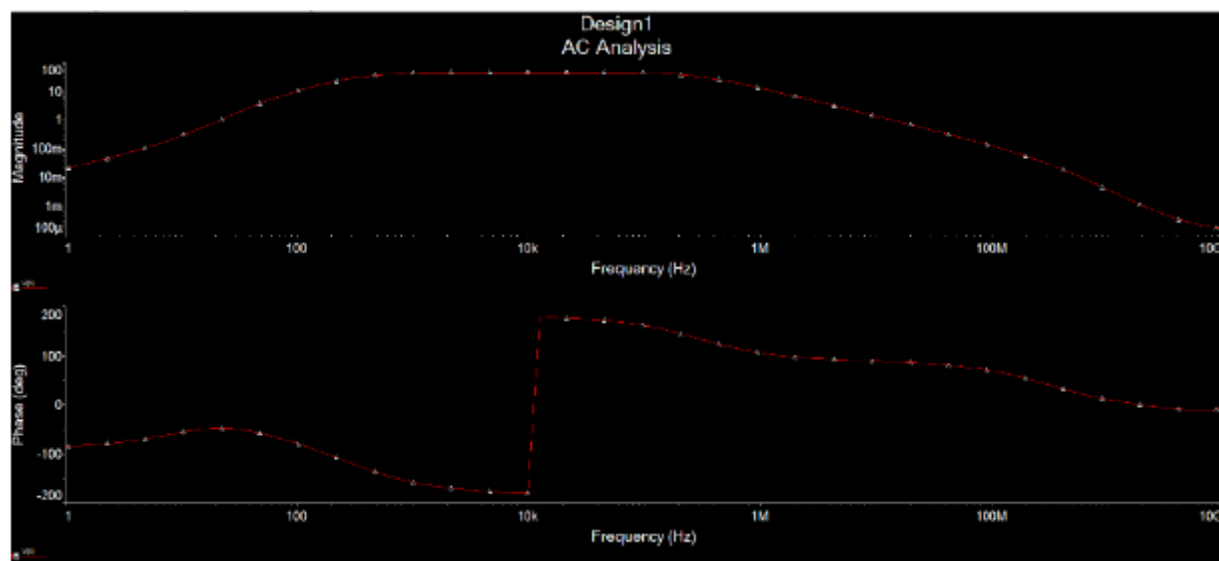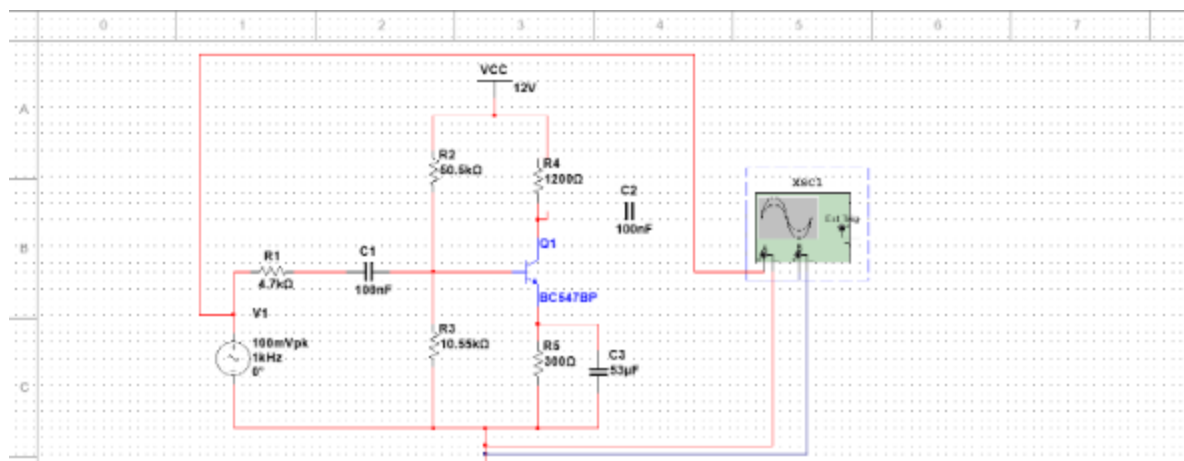

The End